

Electrical System

Tuesday, 27 February 2024 7:52 am

$$\begin{aligned}
 & \text{Circuit Components: } R = 1\Omega, L = 1H, C = 1\text{mf} \\
 & \text{Initial Conditions: } i(t) \rightarrow i(t), v_c(t) \rightarrow v_c(t) \\
 & \text{Laplace Transform: } \mathcal{L}\{v_R(t)\} = R i(t) \quad (1) \\
 & \mathcal{L}\{v_L(t)\} = L \frac{di(t)}{dt} \quad (2) \\
 & \mathcal{L}\{v_C(t)\} = \frac{1}{C} \int i(t) dt + v_c(t) \quad (3) \\
 & \text{Voltage Law: } V_R(s) = R I(s) \quad (4) \\
 & V_L(s) = L s I(s) \quad (5) \\
 & V_C(s) = \frac{I(s)}{Cs} \quad (6) \\
 & \text{Constant: } \boxed{R, L, C} \\
 & \boxed{\bar{E} = IR} \\
 & \boxed{V = IR} \\
 & \boxed{E_{ext} = IR}
 \end{aligned}$$

$$\begin{aligned}
 & \text{Circuit Diagram: } V(t) \rightarrow i(t) \rightarrow R \rightarrow L \rightarrow C \rightarrow V(t) \\
 & G(s) = \frac{V_o(s)}{V_i(s)} \rightarrow V_R(s), V_L(s), V_C(s), I(s) \\
 & G(s) = \frac{I(s)}{V_i(s)} \\
 & \text{Steps:} \\
 & (1) KVL / Mesh / Node \\
 & (2) Laplace Transform \\
 & (3) Linear Algebra (sub, elim, Cramer's) \\
 & (4) Solve for G(s)
 \end{aligned}$$

$$\begin{aligned}
 G(s) &= \frac{I(s)}{V_i(s)} \quad (1) \\
 -V_i(t) &= V_R(t) + V_L(t) + V_C(t) \\
 -V_i(t) &= R i(t) + \frac{1}{C} \int i(t) dt + L \frac{di(t)}{dt}
 \end{aligned}$$

$$(2) V_i(s) = R I(s) + \frac{1}{Cs} I(s) + L s I(s)$$

$$(3) V_i(s) = I(s) \left(R + \frac{1}{Cs} + Ls \right)$$


$$\begin{aligned}
 (4) \quad & V_i(s) = I(s) \left(\frac{RCs + 1 + LCs^2}{Cs} \right) \frac{1}{V_i(s)} \cdot \frac{Cs}{RCs + 1 + LCs^2} \\
 \frac{I(s)}{V_i(s)} &= \frac{Cs}{LCs^2 + RCs + 1} \quad \text{if } C = 4 \\
 & L = 3 \\
 & R = 2 \\
 & = \frac{4s}{2s^2 + 8s + 1} \quad \boxed{\frac{4s}{2s^2 + 8s + 1}} \rightarrow \frac{V_i(s)}{I(s)} = \frac{4s}{2s^2 + 8s + 1}
 \end{aligned}$$

$$\begin{aligned}
 & \boxed{\frac{V_i(s)}{I(s)} = \frac{4s}{2s^2 + 8s + 1}} \rightarrow I(s) \\
 & \frac{V_R(s)}{V_i(s)} = ?, \quad \frac{V_L(s)}{V_i(s)} = ?, \quad \frac{V_C(s)}{V_i(s)} = ?
 \end{aligned}$$


$$\begin{aligned}
 & V_R(s) = R I(s) \quad (2) \\
 & I(s) = \frac{V_R(s)}{R} \\
 & V_L(s) = L s I(s) \quad (5) \\
 & I(s) = \frac{V_L(s)}{Ls} \\
 & V_C(s) = \frac{I(s)}{Cs} \quad (6) \\
 & I(s) = Cs V_C(s)
 \end{aligned}$$

$$\frac{I(s)}{V_i(s)} = \frac{4s}{12s^2 + 8s + 1}$$

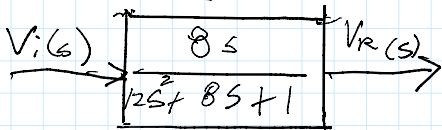
$$R \left[\frac{V_R(s)}{V_i(s)} = \frac{4s}{12s^2 + 8s + 1} \right] R = 2 = \frac{8s}{12s^2 + 8s + 1}$$



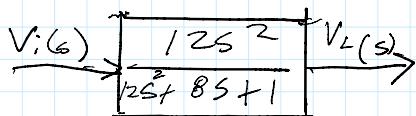
$$L \left\{ \frac{V_L(s)}{Ls V_i(s)} = \frac{4s}{12s^2 + 8s + 1} \right\} L \sim 3 = 12s^2$$


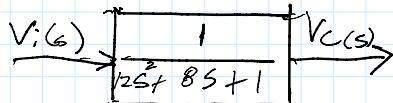
$$\frac{1}{Cs} \left\{ \frac{Cs V_C(s)}{V_i(s)} = \frac{4s}{12s^2 + 8s + 1} \right\} \frac{1}{Cs} \sim 4$$



Block diagram Application

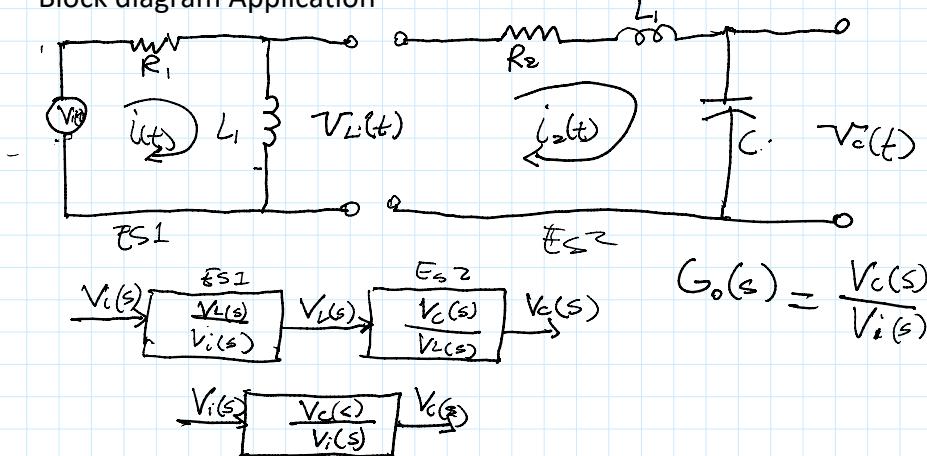

$$R_1 = R_2 = 1, L_1 = L_2 = 2, C = 3$$


$$G_1(s) = \frac{V_L(s)}{V_i(s)}$$

$$\textcircled{1} \quad V_i(t) = R i(t) + L \frac{di(t)}{dt} \quad \textcircled{2} \quad V_L(t) = L \frac{di(t)}{dt}$$

$$\textcircled{1} \quad V_i(s) = R I(s) + L s I(s) \quad \textcircled{2} \quad V_L(s) = L s I(s)$$

$$\frac{V_L(s)}{V_i(s)} = \frac{L s I(s)}{I(s)[L s + R]} = \frac{2s}{2s + 1}$$
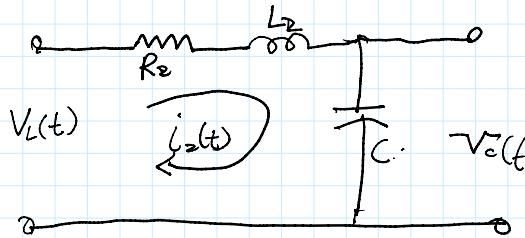
$$G_1(s) = \frac{V_L(s)}{V_i(s)} = \frac{2s}{2s + 1}$$



$$G_2(s) = \frac{V_C(s)}{V_L(s)}$$


$$\textcircled{1} \quad V_L(t) = R_2 i_2(t) + L_2 \frac{di_2(t)}{dt} + \frac{1}{C} \int i_2(t) dt \quad \textcircled{2} \quad V_C(t) = \frac{1}{C} \int i_2(t) dt$$

$$\textcircled{1} \quad V_L(s) = R_2 I_2(s) + L_2 s I_2(s) + \frac{1}{Cs} I_2(s) \quad \textcircled{2} \quad V_C(s) = \frac{1}{Cs} I_2(s)$$

$$\begin{aligned} \frac{V_C(s)}{V_L(s)} &= \frac{\frac{I_2(s)}{Cs}}{\frac{I_2(s)}{Cs} [L_2 s + R_2 + \frac{1}{Cs}]} \\ &= \frac{1}{L_2 Cs^2 + R_2 Cs + 1} = \frac{1}{6s^2 + 3s + 1} \end{aligned}$$


$$G_2(s) = \frac{V_L(s)}{\frac{1}{6s^2 + 3s + 1} V_C(s)}$$

$$G_o(s) = \frac{V_C(s)}{V_L(s)}$$

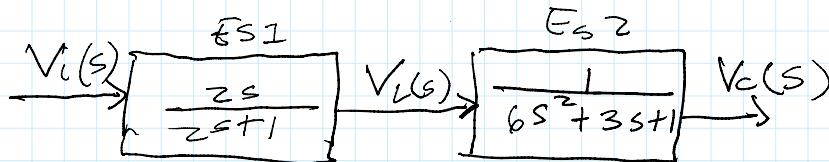

$$\frac{V_L(s)}{\frac{zs}{(zs+1)(6s^2+3s+1)} V_C(s)}$$

Example 3:

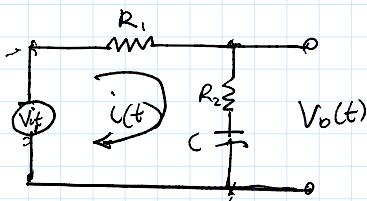

$$G(s) = \frac{V_C(s)}{V_L(s)}$$


$$V_i(t) = V_{R_1}(t) + V_{R_2}(t) + V_C(t) \quad \textcircled{2} \quad V_C(t) = V_{R_2}(t) + V_C(t)$$

$$\frac{V_C(s)}{V_L(s)} = \frac{R_2 I_2(s) + \frac{E(s)}{Cs}}{R_1 I_1(s) + R_2 I_2(s) + \frac{E(s)}{Cs}}$$

$$V_{R_2}(t) = V_C(t) - V_{R_2}(t)$$

$$\frac{V_o(s)}{V_i(s)} = \frac{\frac{R_2(s+1)}{Cs}}{\frac{R_1(s+R_2(s+1))}{Cs}}$$

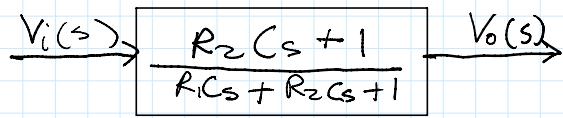
$$\frac{V_o(s)}{V_i(s)} = \frac{R_2(s+1)}{R_1(s+R_2(s+1))}$$




$$\frac{V_{R_2}(s)}{V_i(s)} = ?$$

$$\frac{V_{R_2}(s) + V_C(s)}{V_i(s)} = \frac{R_2(s+1)}{R_1(s+R_2(s+1))}$$

$$\frac{V_{R_2}(s) + V_C(s)}{V_i(s)} = \frac{R_2(s+1)}{R_1(s+R_2(s+1))} - \frac{\frac{1}{Cs} \frac{I(s)}{s}}{\cancel{s}[R_1(s+R_2(s+1))]}$$

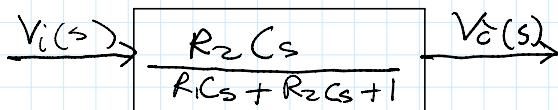

Example 4:

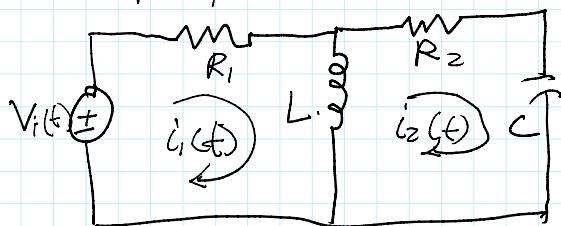

$$G(s) = \frac{I_2(s)}{V(s)}$$

$$\text{if: } R_1 = R_2 = 1$$

$$L = 2$$

$$C = 3$$

(1) $V_i(t) = R_1 i_1(t) + L \frac{d i_1(t)}{dt} - L \frac{d i_2(t)}{dt}$

(2) $0 = L i_2(t) + R_2 i_2(t) + C i_2(t) - L i_1(t)$

$$V_i(s) = I_1(s) [Ls + R_1] - Ls I_2(s)$$

$$0 = I_2(s) \left[Ls + R_2 + \frac{1}{Cs} \right] - Ls I_1(s)$$

$$I_2(s) \xrightarrow{\begin{bmatrix} Ls+R_1 & V_i(s) \\ -Ls & 0 \end{bmatrix}} = \frac{0 - (-\cdot Ls V_i(s))}{\underbrace{(L^2 s^3 + R_2 C L s^2 + Ls + R_1 L C s^2 + R_1 R_2 (s + R_1))}_{Cs}}$$

$$I_2(s) = \frac{L C s^2 V_i(s)}{L^2 s^3 - R_2 C L s^2 + Ls + R_1 L C s^2 + R_1 R_2 (s + R_1)}$$

$$\begin{aligned} \frac{I_2(s)}{V_i(s)} &= \frac{L C s^2}{L^2 s^3 - R_2 C L s^2 + Ls + R_1 L C s^2 + R_1 R_2 (s + R_1)} \\ &= \frac{(2)(3)s^2}{(2)^2(3)s^3 - (1)(3)(2)s^2 + 2s + (2)(3)s^2 + (1)(1)(3)s + 1} \\ &= \frac{6s^2}{12s^3 - 6s^2 + 2s + 6s^2 + 3s + 1} \\ &= \frac{6s^2}{12s^3 + 5s + 1} \end{aligned}$$

$$\frac{V_i(s)}{12s^3 + 5s + 1} \xrightarrow{6s^2} I_2(s)$$